

---

# Simulation and PCB Designing of Buck Converter

Name- Mouni Rishitha Perika

Roll No: 234102110

21<sup>st</sup> Aug 2024


---

## Objective:

The objective of experiment is to familiarize the student with MATLAB/SIMULINK and important simulation settings. For this a buck converter with the following parameter has to be designed and simulated.

|                            |         |
|----------------------------|---------|
| Input Voltage              | 24 V    |
| Output Voltage             | 12 V    |
| Output power               | 100 W   |
| Switching Frequency        | 100 kHz |
| Ripple in inductor current | 25%     |
| Ripple in output voltage   | 0.1%    |

## Circuit Diagram:

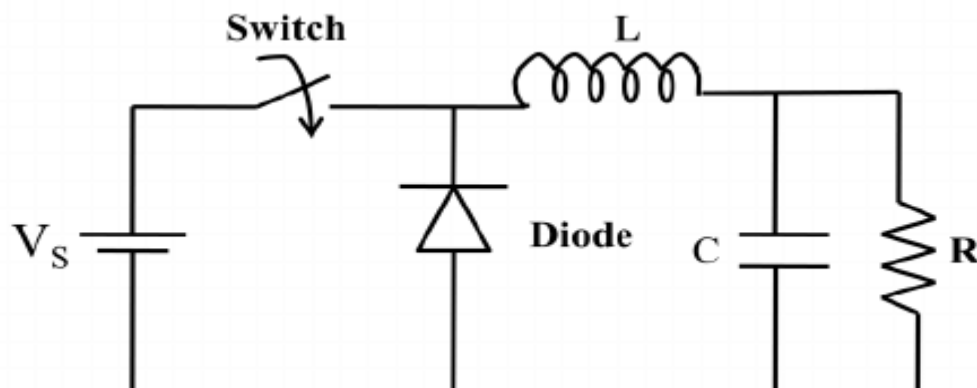

## Design Procedure and Calculation Output Voltage:

The value of inductance can be found by using the below expression

$$L = \frac{D(1-D)V_{in}}{\Delta I_L \cdot f_{sw}} \quad (1)$$

$$V_o = D \cdot V_{in} \quad (2)$$

Inductor value comes out to be= 28.8  $\mu$ H

The capacitance value can be calculated by using the following expression

$$C = \frac{\Delta I_L}{8f_{sw} \Delta V_C} \quad (3)$$

The capacitance value comes out to be approximately= 217  $\mu$ F.

Transfer Functions of Buck Converter:


$$\frac{V_o(s)}{V_{in}(s)} = \frac{V_{in}}{s^2 LC + sL + \frac{L}{R}}$$

$$\frac{V_o(s)}{d(s)} = \frac{D}{s^2 LC + sL + \frac{L}{R}}$$

### Code for Bode plot of boost converter:


```
vin=48;
D=0.5;
R=5;
fs=50e3;
C=200e-6;
L=0.125e-3;
%H=v0/d% H=tf(vin,[L*C,L/R,1]); display(H);
figure(1) margin(H); bode(H) grid
[Gm,Pm,Wcg,Wcp] = margin(H);
[p,z] = pzmap(H);
%G=vin/vo% G=tf(D,[L*C,L/R,1]);
display(G); figure(2) bode(G) margin(G); grid
[Gm,Pm,Wcg,Wcp] = margin(G);
[p,z] = pzmap(G);
```

### MATLAB/SIMULINK SIMULATION

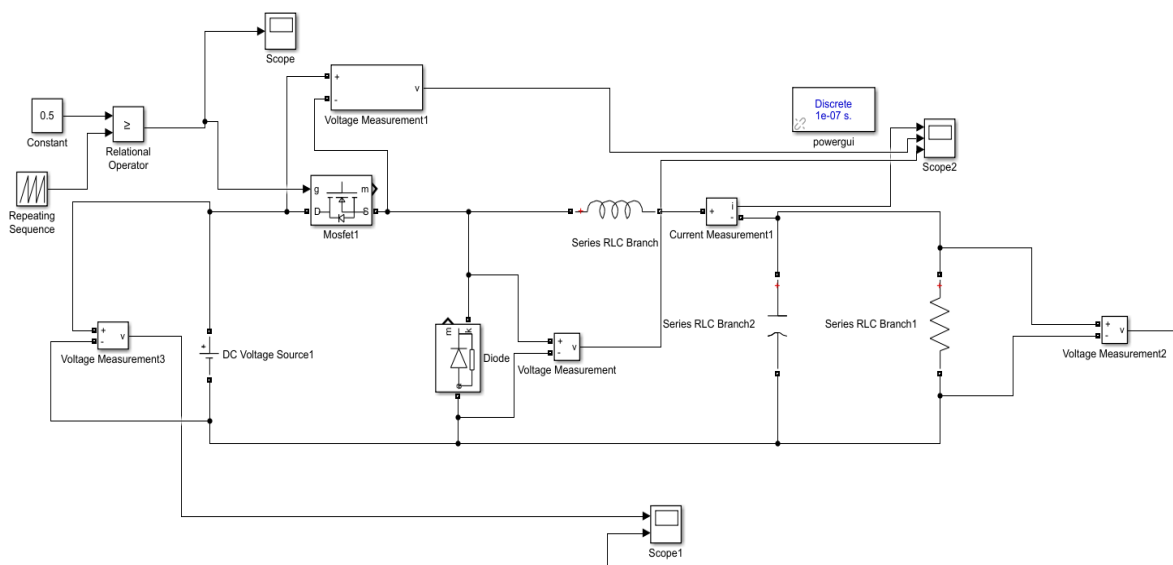


## SIMULATED WAVEFORMS:


### Input Voltage

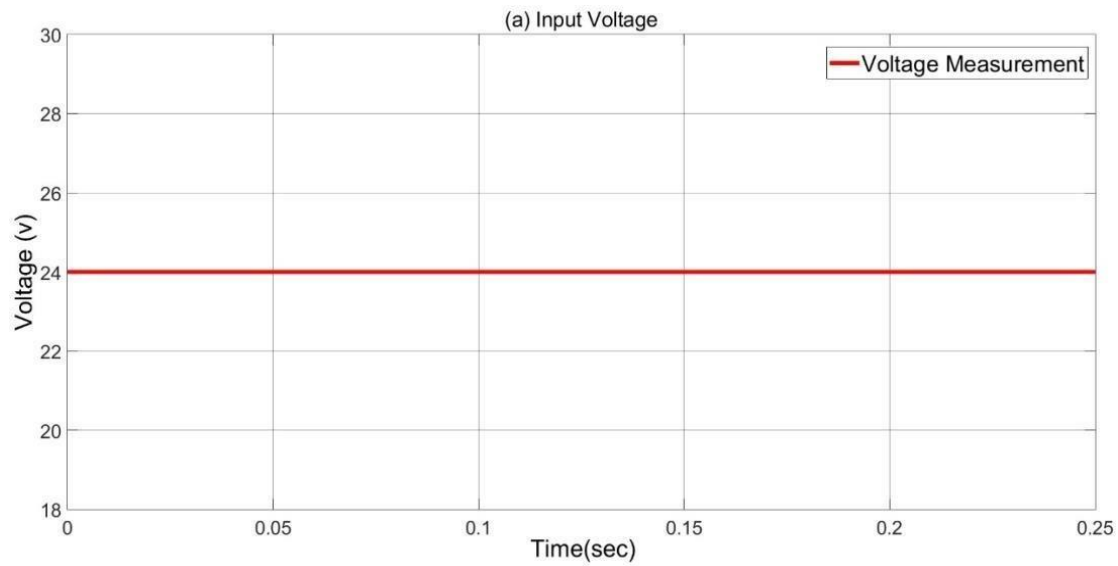


### Inductor current

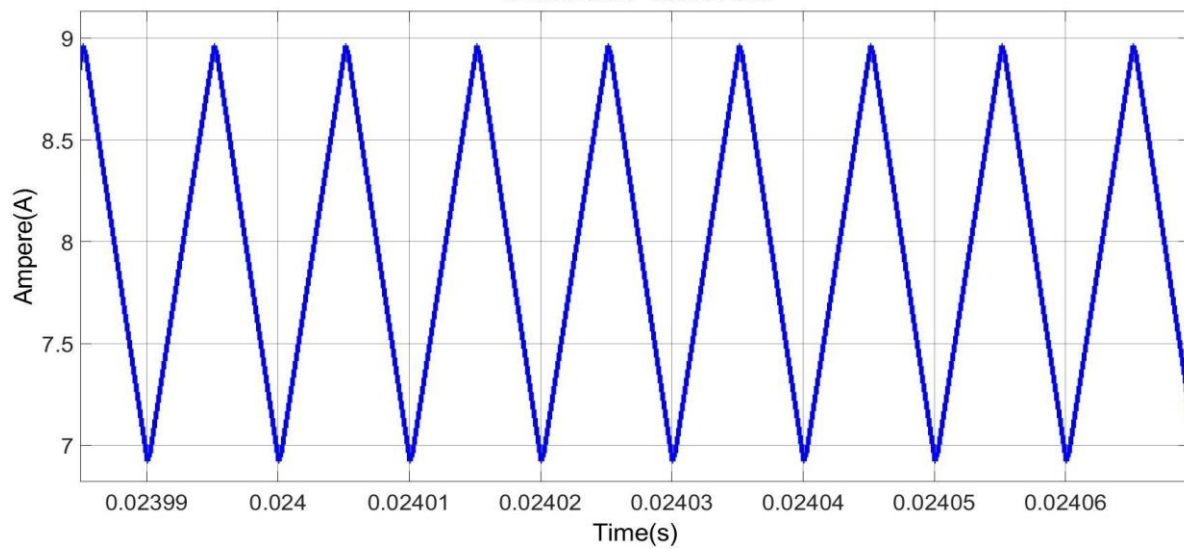


### Switching signal

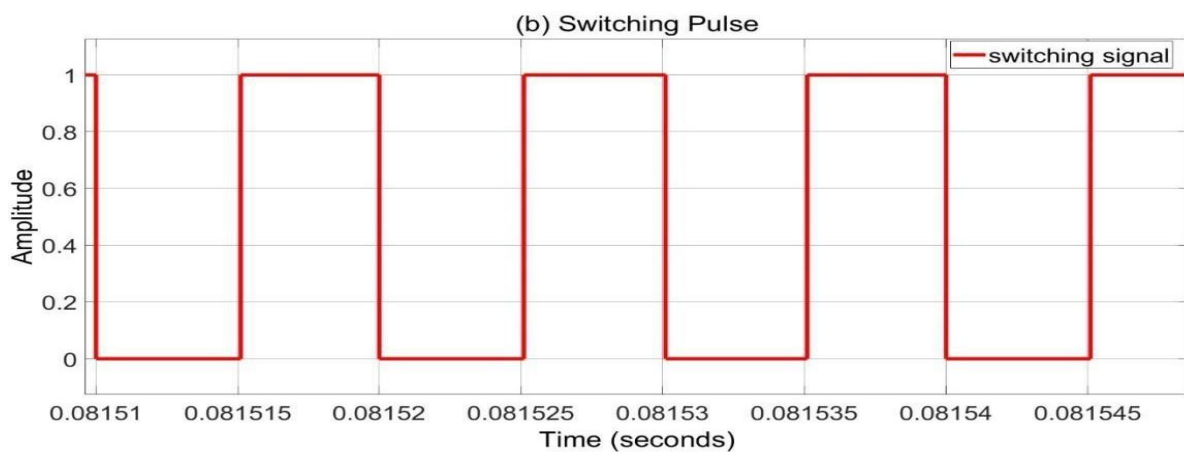


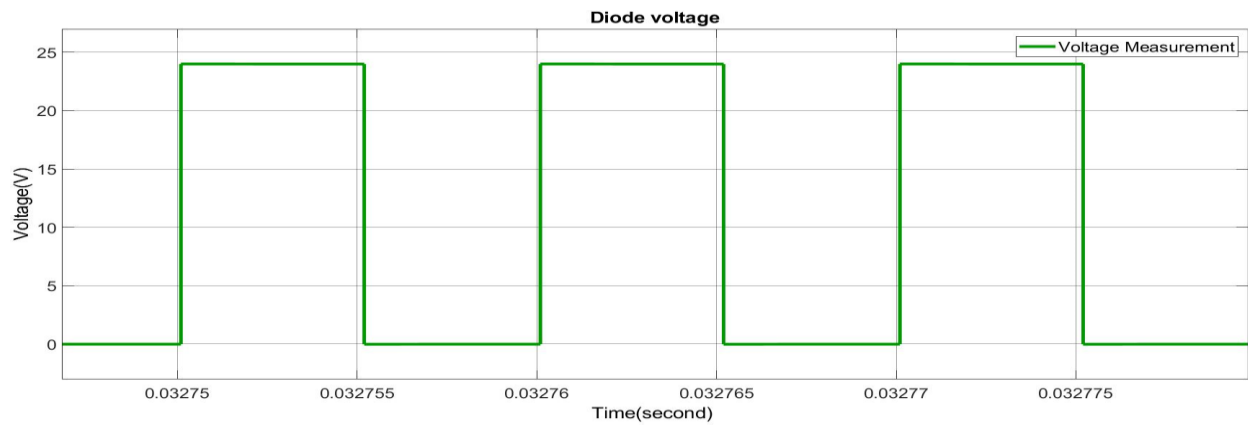



**Output Voltage**

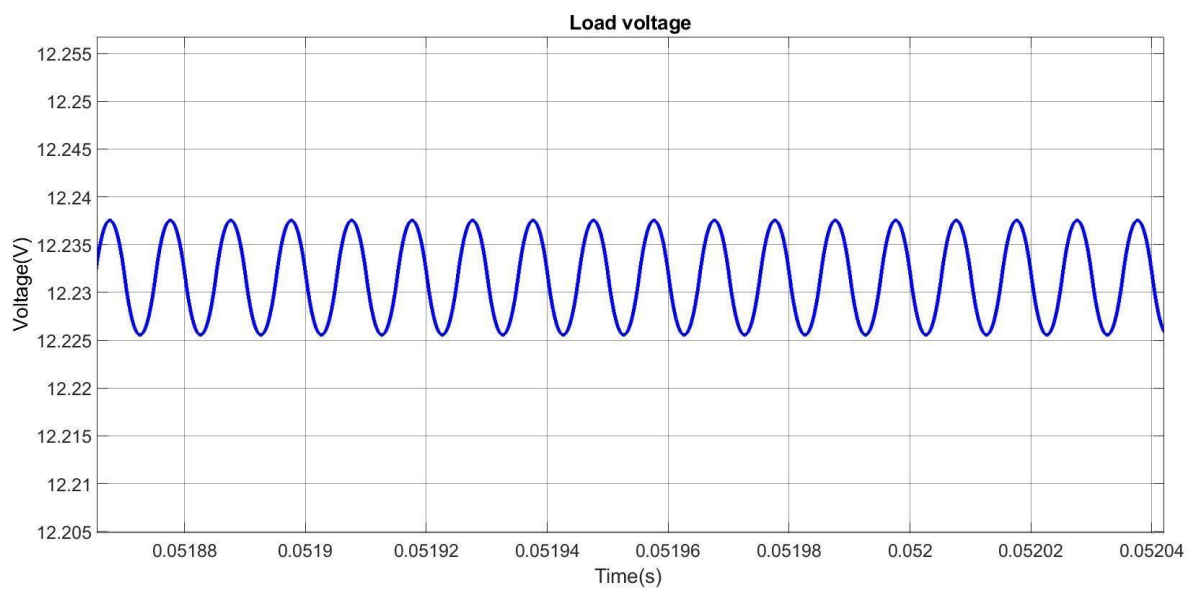


**Voltage across switch**

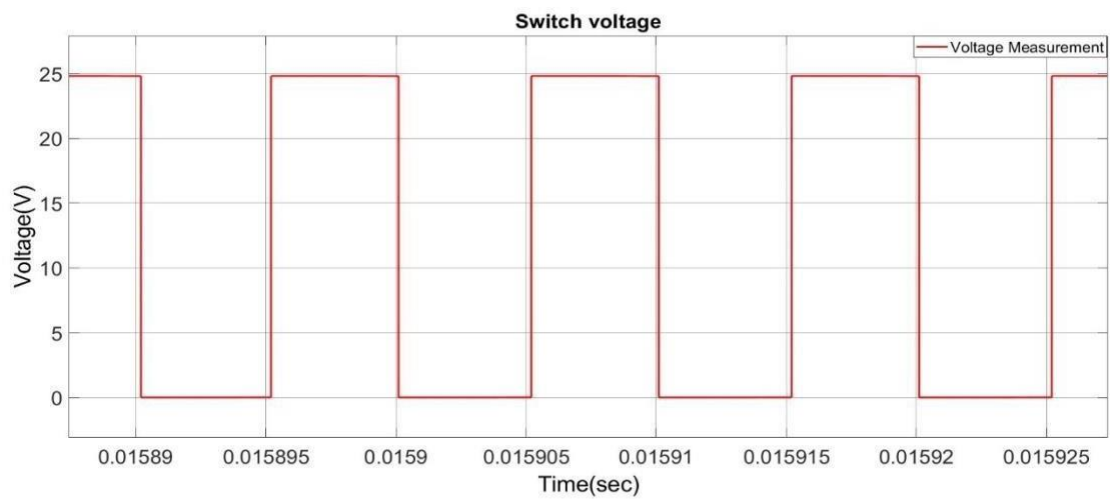

## Bode Plots of Buck converter:

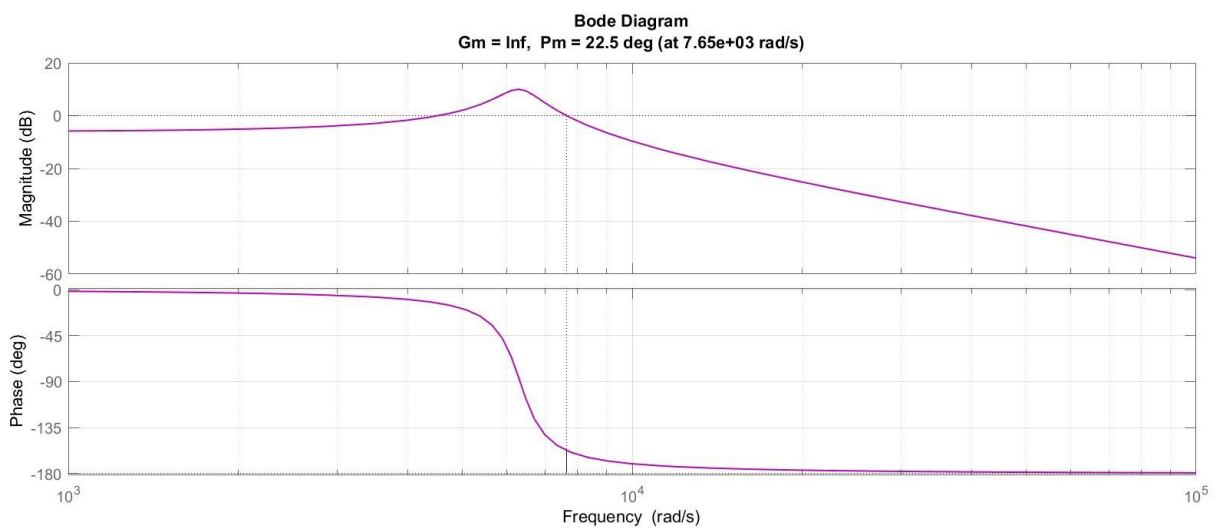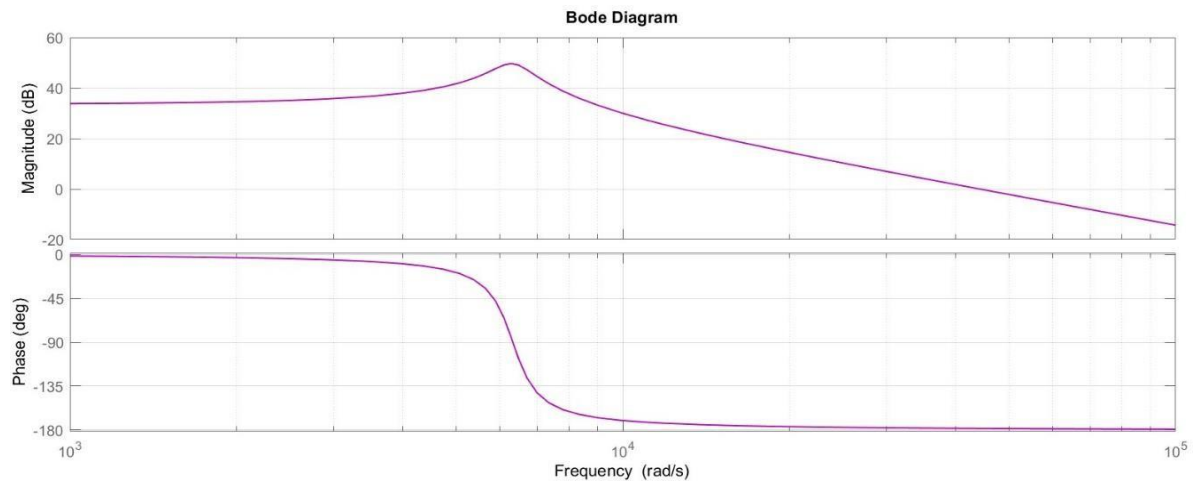

## Simulation configuration parameters:

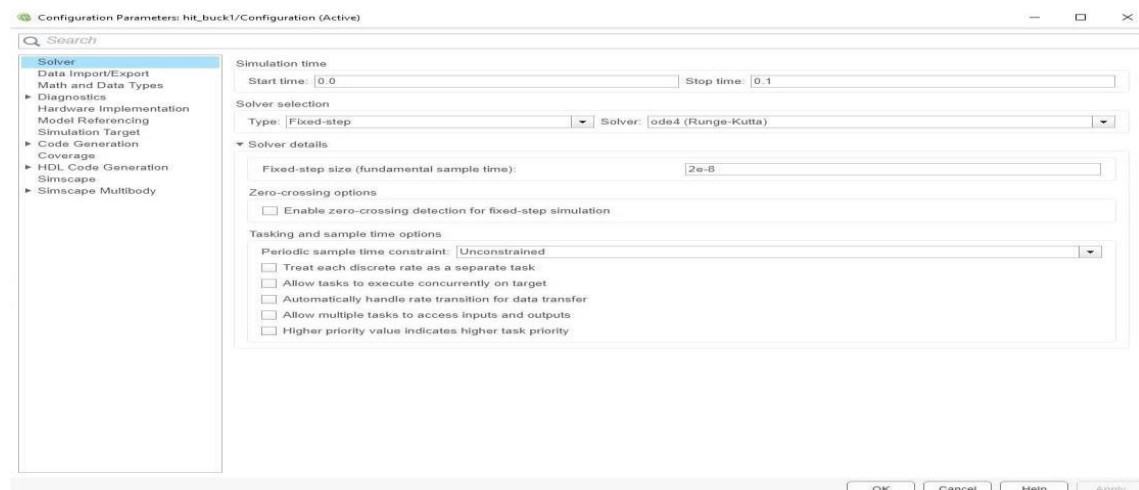

```

>> bodeplotbuck
H =
-----
          48
2.5e-08 s^2 + 2.5e-05 s + 1

Continuous-time transfer function.
Model Properties

p =
      1.0e+03 *
      -0.5000 + 6.3048i
      -0.5000 - 6.3048i

z =
      0x1 empty double column vector

G =
-----
          0.5
2.5e-08 s^2 + 2.5e-05 s + 1

Continuous-time transfer function.
Model Properties


p =
      1.0e+03 *
      -0.5000 + 6.3048i
      -0.5000 - 6.3048i

z =
      0x1 empty double column vector


>>

```

## PCB Schematic:

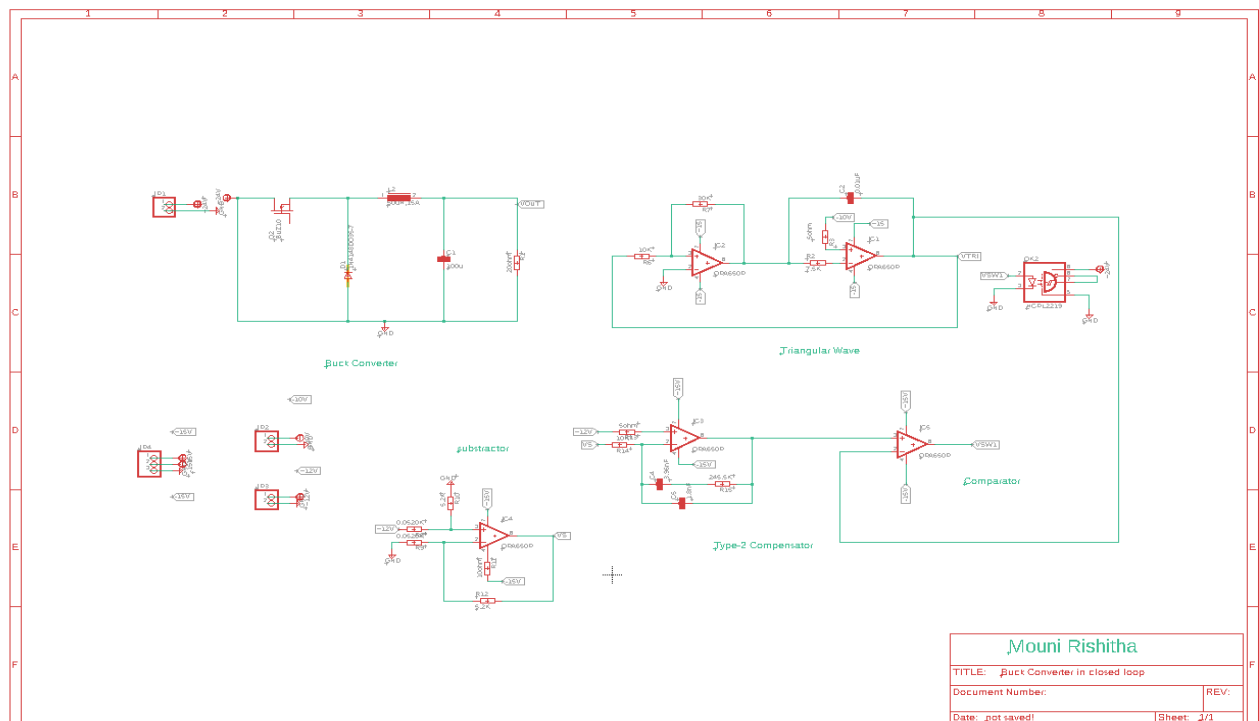

## PCB Board:

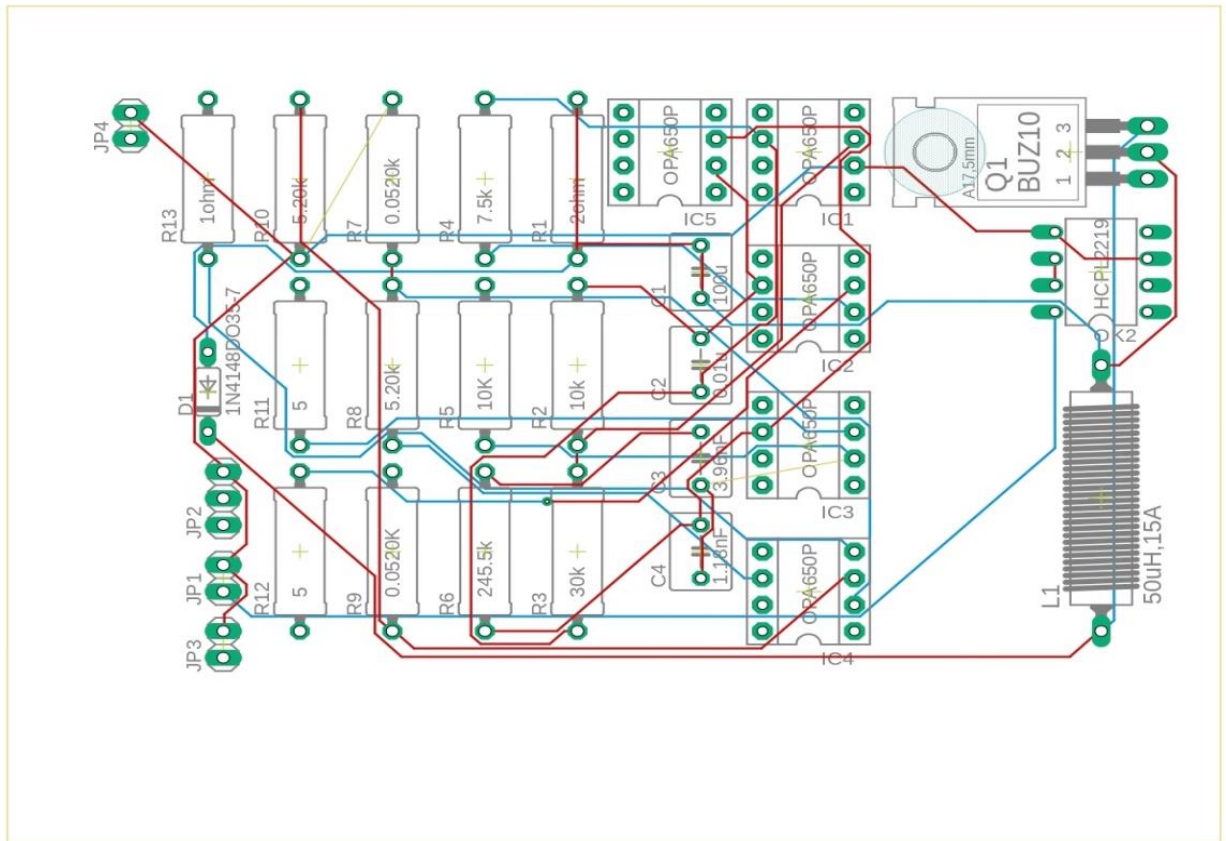

## PCB Manufacturing Diagram:

