
Simulation and PCB Designing of Buck Converter

Name- Mouni Rishitha Perika

Roll No: 234102110


21st Aug 2024

Objective:

The objective of experiment is to familiarize the student with MATLAB/SIMULINK and important simulation settings. For this a buck converter with the following parameter has to be designed and simulated.

Input Voltage	24 V
Output Voltage	12 V
Output power	100 W
Switching Frequency	100 kHz
Ripple in inductor current	25%
Ripple in output voltage	0.1%

Circuit Diagram:

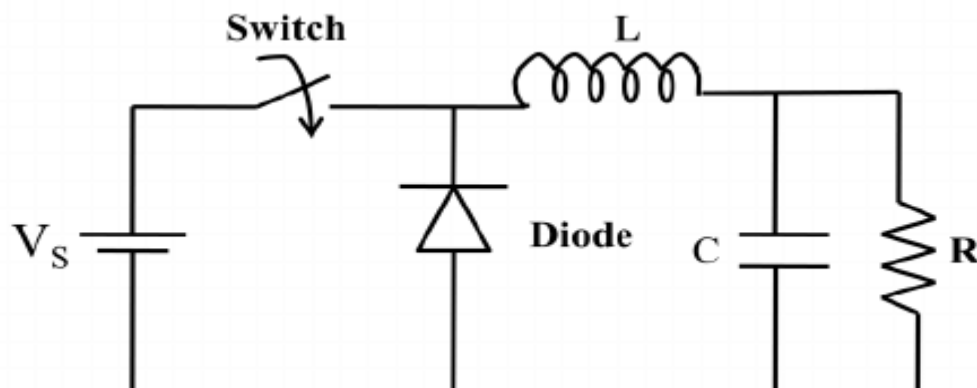

Design Procedure and Calculation Output Voltage:

The value of inductance can be found by using the below expression

$$L = \frac{D(1-D)V_{in}}{\Delta I_L \cdot f_{sw}} \quad (1)$$

$$V_o = D \cdot V_{in} \quad (2)$$

Inductor value comes out to be= 28.8 μ H

The capacitance value can be calculated by using the following expression

$$C = \frac{\Delta I_L}{8f_{sw} \Delta V_C} \quad (3)$$

The capacitance value comes out to be approximately= 217 μ F.

Transfer Functions of Buck Converter:


$$\frac{V_o(s)}{V_{in}(s)} = \frac{V_{in}}{s^2 LC + sL + \frac{L}{R}}$$

$$\frac{V_o(s)}{d(s)} = \frac{D}{s^2 LC + sL + \frac{L}{R}}$$

Code for Bode plot of boost converter:


```
vin=48;
D=0.5;
R=5;
fs=50e3;
C=200e-6;
L=0.125e-3;
%H=v0/d% H=tf(vin,[L*C,L/R,1]); display(H);
figure(1) margin(H); bode(H) grid
[Gm,Pm,Wcg,Wcp] = margin(H);
[p,z] = pzmap(H);
%G=vin/vo% G=tf(D,[L*C,L/R,1]);
display(G); figure(2) bode(G) margin(G); grid
[Gm,Pm,Wcg,Wcp] = margin(G);
[p,z] = pzmap(G);
```

MATLAB/SIMULINK SIMULATION

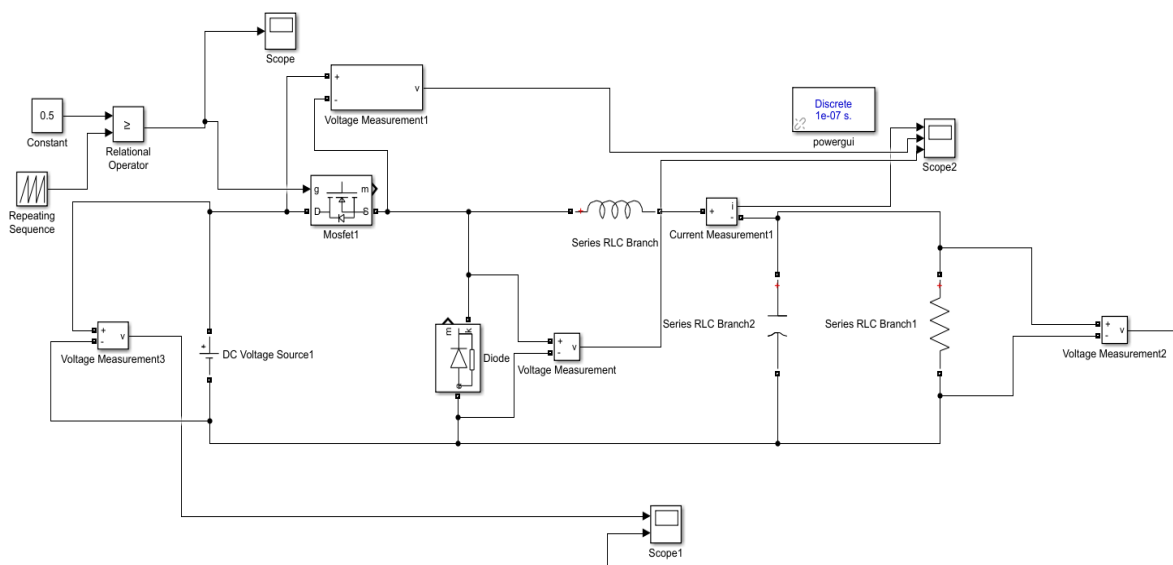


SIMULATED WAVEFORMS:


Input Voltage

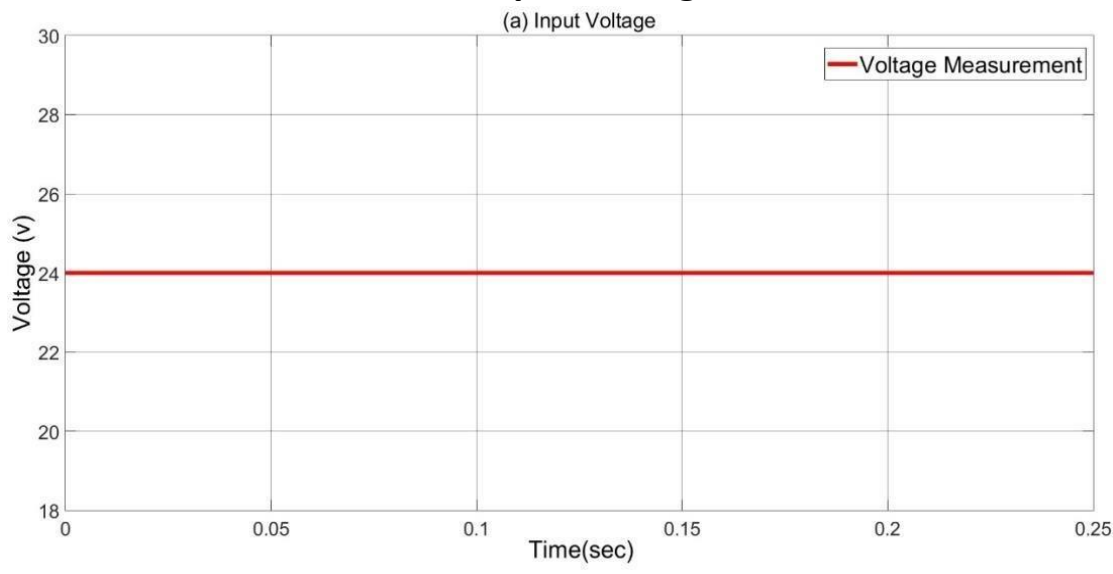


Inductor current

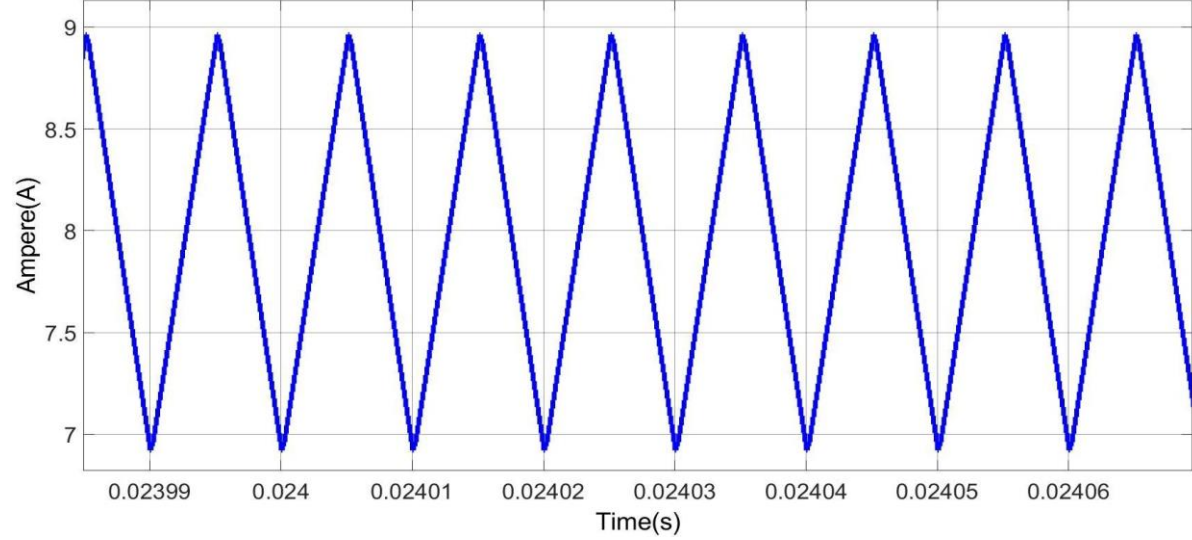


Switching signal

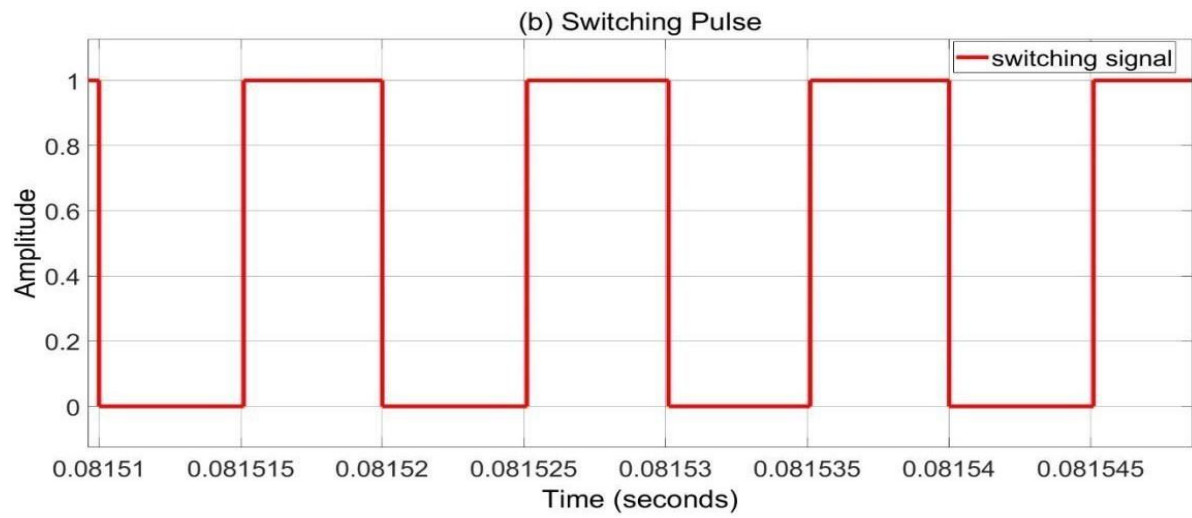


Output Voltage

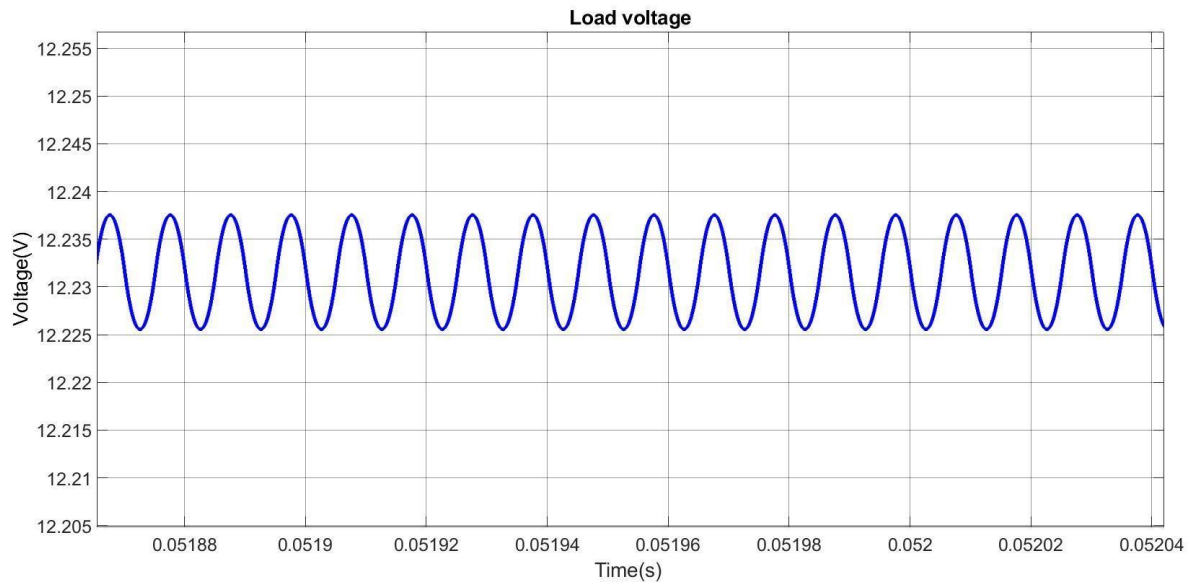


Voltage across switch

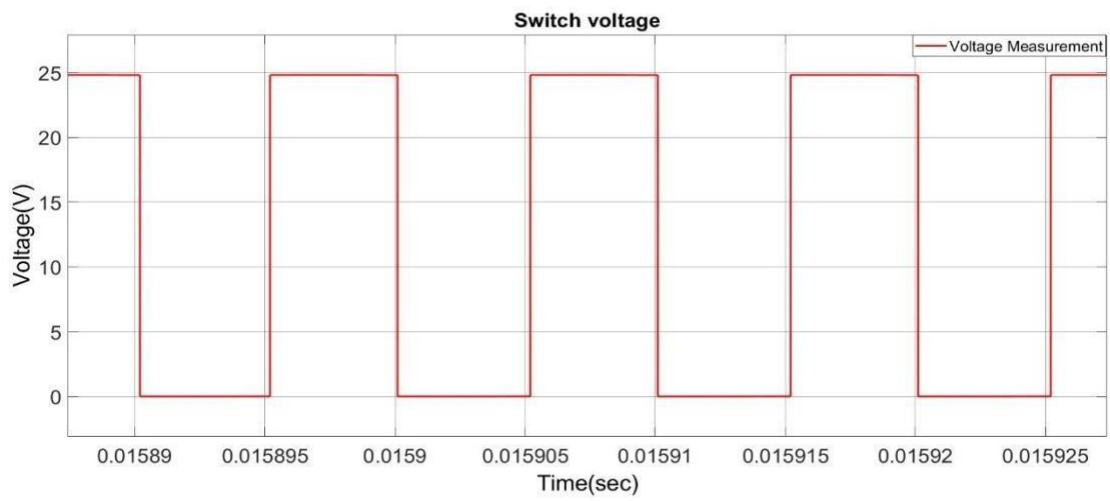


Voltage across diode

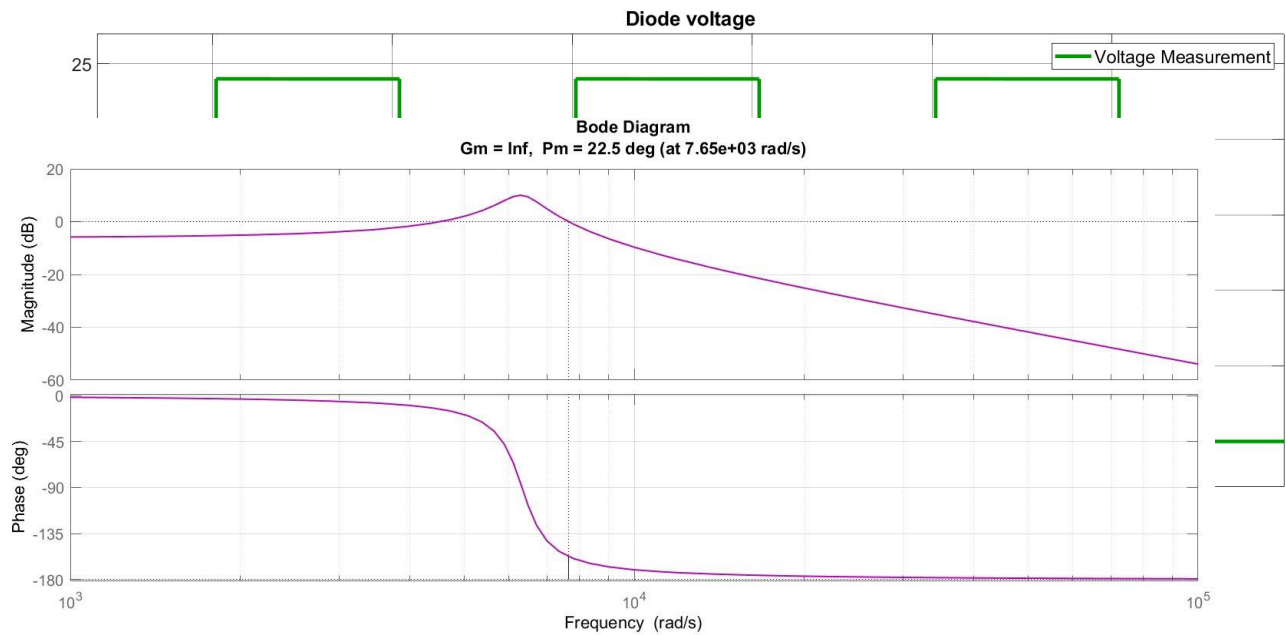

Bode Plots of Buck converter:

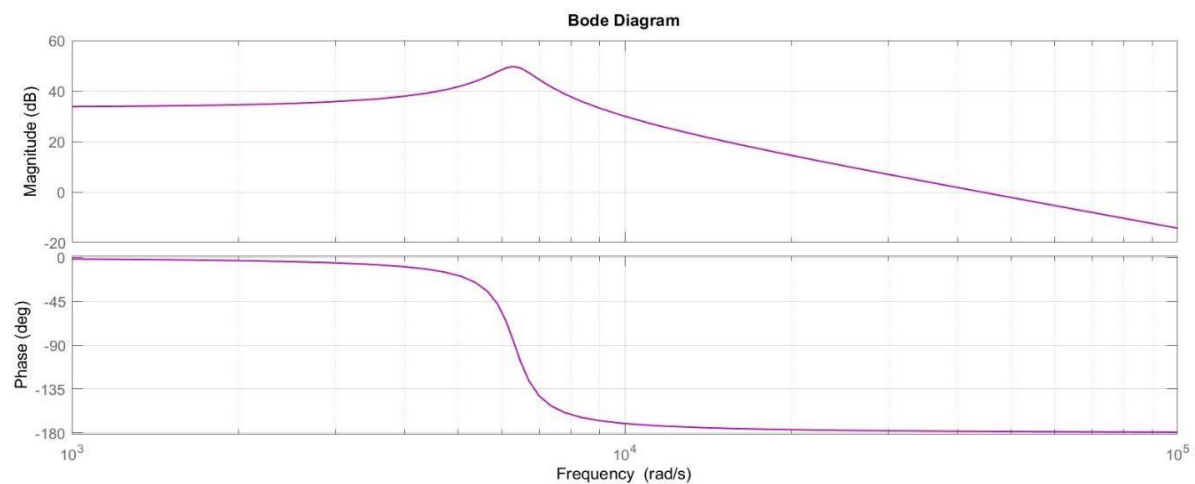

Simulation configuration parameters:

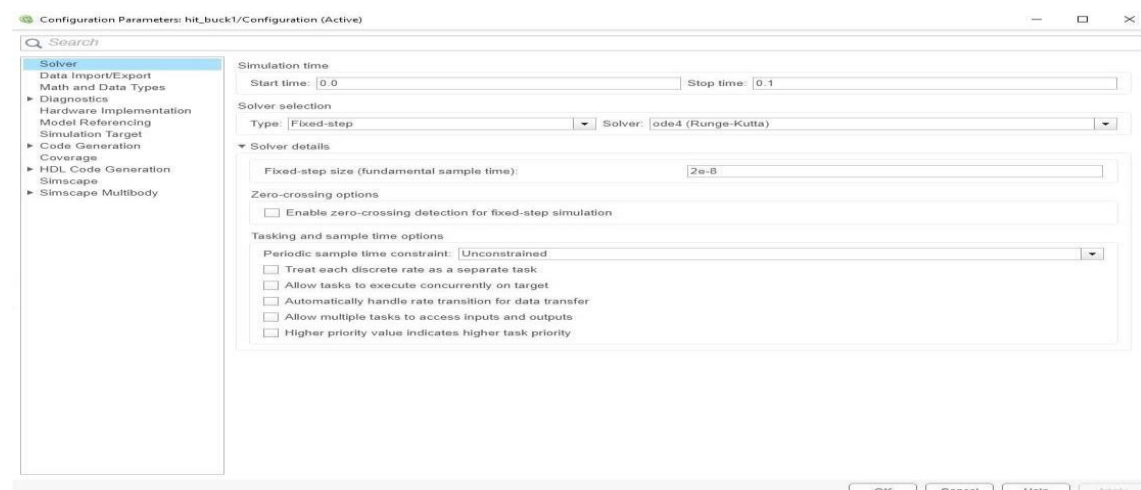

```
>> bodeplotbuck
```

```
H =
```

$$\frac{48}{2.5e-08 s^2 + 2.5e-05 s + 1}$$

Continuous-time transfer function.
Model Properties

```
p =
```

$$1.0e+03 * \\ -0.5000 + 6.3048i \\ -0.5000 - 6.3048i$$

```
z =
```

0×1 empty double column vector

```
G =
```

$$\frac{0.5}{2.5e-08 s^2 + 2.5e-05 s + 1}$$

Continuous-time transfer function.
Model Properties

```
p =
```


$$1.0e+03 * \\ -0.5000 + 6.3048i \\ -0.5000 - 6.3048i$$

```
z =
```


0×1 empty double column vector

```
>>
```

PCB Schematic:

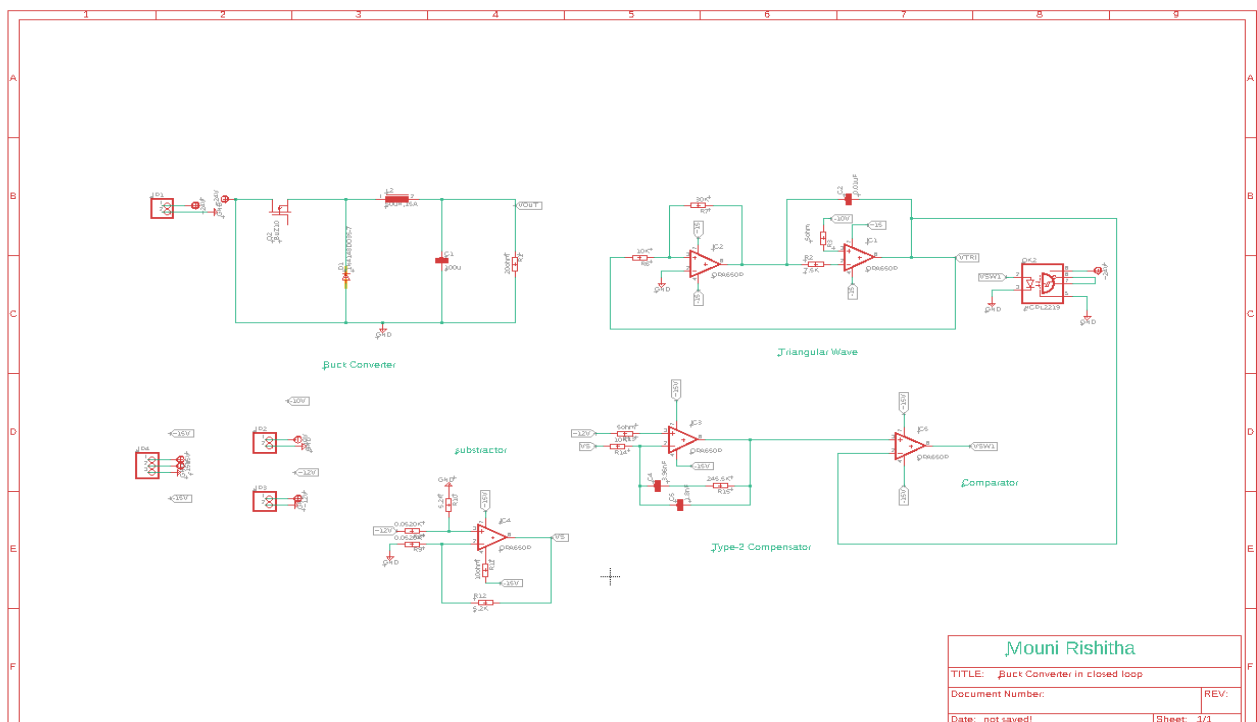

PCB Board:

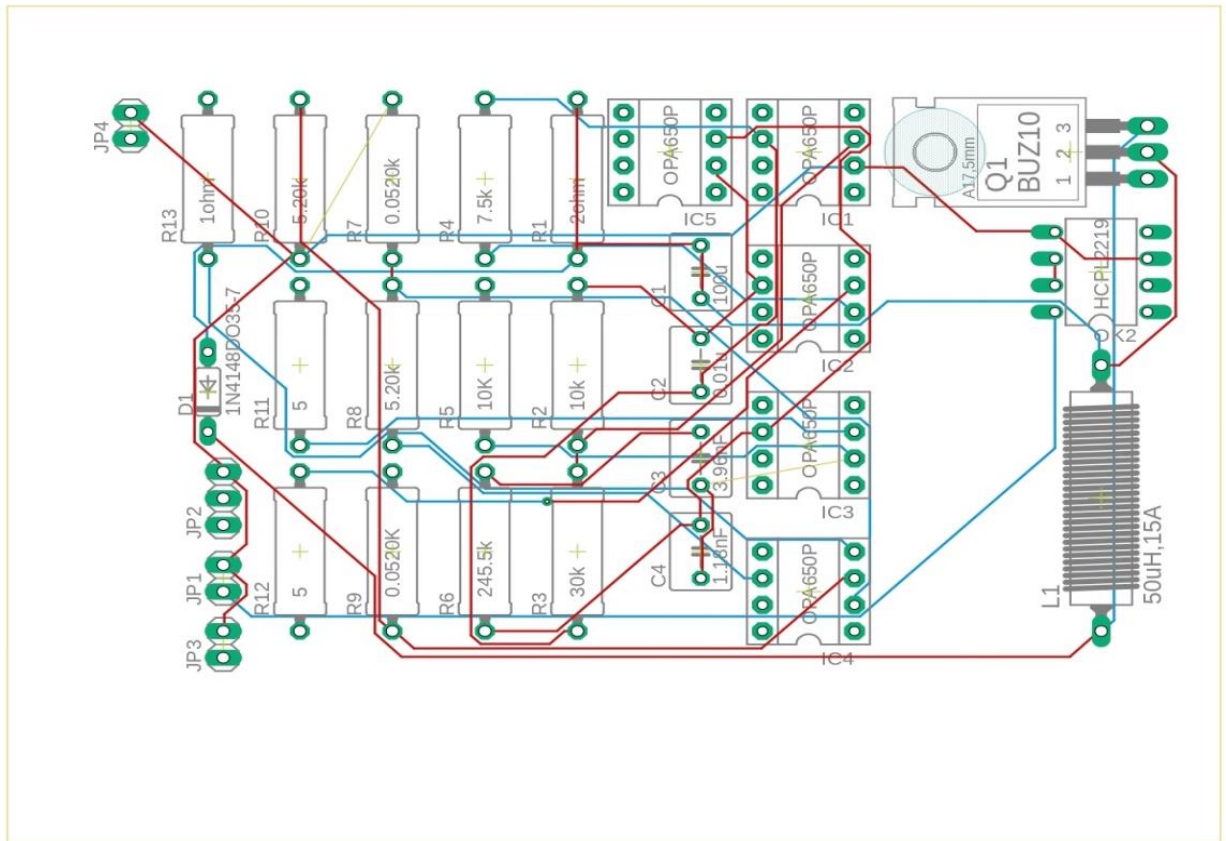

PCB Manufacturing Diagram:

